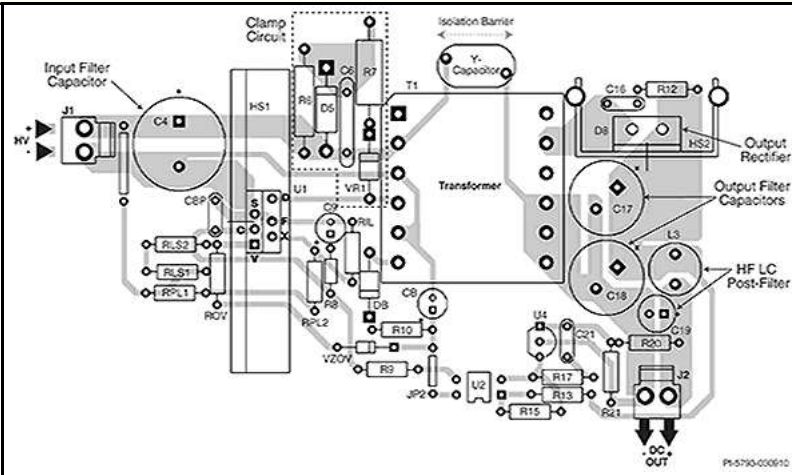


Board Layout Recommendations



Click on the "Show me" icon to highlight relevant areas on the sample layout.

	Description	Show Me
1	Minimize loop area formed by drain, clamp and transformer	
2	Bias winding and bias capacitor are a power connection and therefore returned to Kelvin connection at SOURCE pin	
3	V and X pin node areas minimized, line sensing (R1 & R2) and power limiting (R3 & R4) close to device. Connections to V and X pin nodes should be away from noisy switching nodes (drain, clamp and bias)	
4	Place CONTROL pin decoupling capacitor directly across CONTROL and SOURCE pins	
5	Y capacitor connected between output RTN and B+	
6	Minimize loop area formed by secondary winding, the output diode and the output filter capacitor	
7	Kelvin connection at SOURCE pins: power and signal currents kept separate	
8	B+ connection of RLS or RPL resistor should be on input side of capacitor to prevent switching noise injection	